

**UNIVERSITY OF BUEA**

P.O. Box 63.

Buea, South West Region

CAMEROON

Tel: (273)33322134/33322690

Fax: (273)33322272



**REPUBLIC OF CAMEROON**

Peace-Work-Fatherland

**FACULTY OF ENGINEERING AND TECHNOLOGY**

**DEPARTEMENT OF COMPUTER ENGINEERING**

**COURSE : COMPUTER ARCHITECTURE. CEF 250**

**COURSE COORDINATOR: DR VALERY NKEMENI**



PROJECT TITLE :

**BUILDING A 16 BIT MICRO-  
COMPUTER**

**Group 27 Members:**

1. KAMCHE YANN ARNAUD-**FE21A208**
2. AHOUMO TEMATEU ROXANE PHILIPINE-**FE21A128**
3. NTUI RAOUL NTUI NJOCK-**FE21A288**
4. CHO WESLEY MUNGO-**FE21A160**
5. DJIALEU TANKOUA KEANE RANDY -**FE21A170**
6. KOUOTOU AHMAD BILAL-**FE21A221**
7. NJOBAM ROSINE DZELAMONYUY-**FE21A396**
8. DJUIKO METSANOU MERIEM TRESOR-**FE21A355**
9. JULIE ENANGA NJOMBE-**FE21A371**

Second Semester Continuous Assessment report, First year (B. ENG) Degree in Computer Engineering.

MAY  
2022

# TABLE OF CONTENTS:

## 1. THE CONTROL UNIT.....1

- The sequence counter.....
- The control logic gate.....
- 4x16 decoder and 3x8 decoder.....
- The 7 flip flops.....
- The PQ generator.....

## 2. THE REGISTERS.....

- The address register.....
- The temporary register.....
- The data register.....
- The program counter.....
- The instruction register.....
- The accumulator.....
- The input register.....
- The output register.....


## 3. THE BUS.....

- 4-Buslines.....

## 4. THE MEMORY.....

## 5. THE ADDER AND LOGIC CIRCUIT.....

# THE 16 BIT COMPUTER

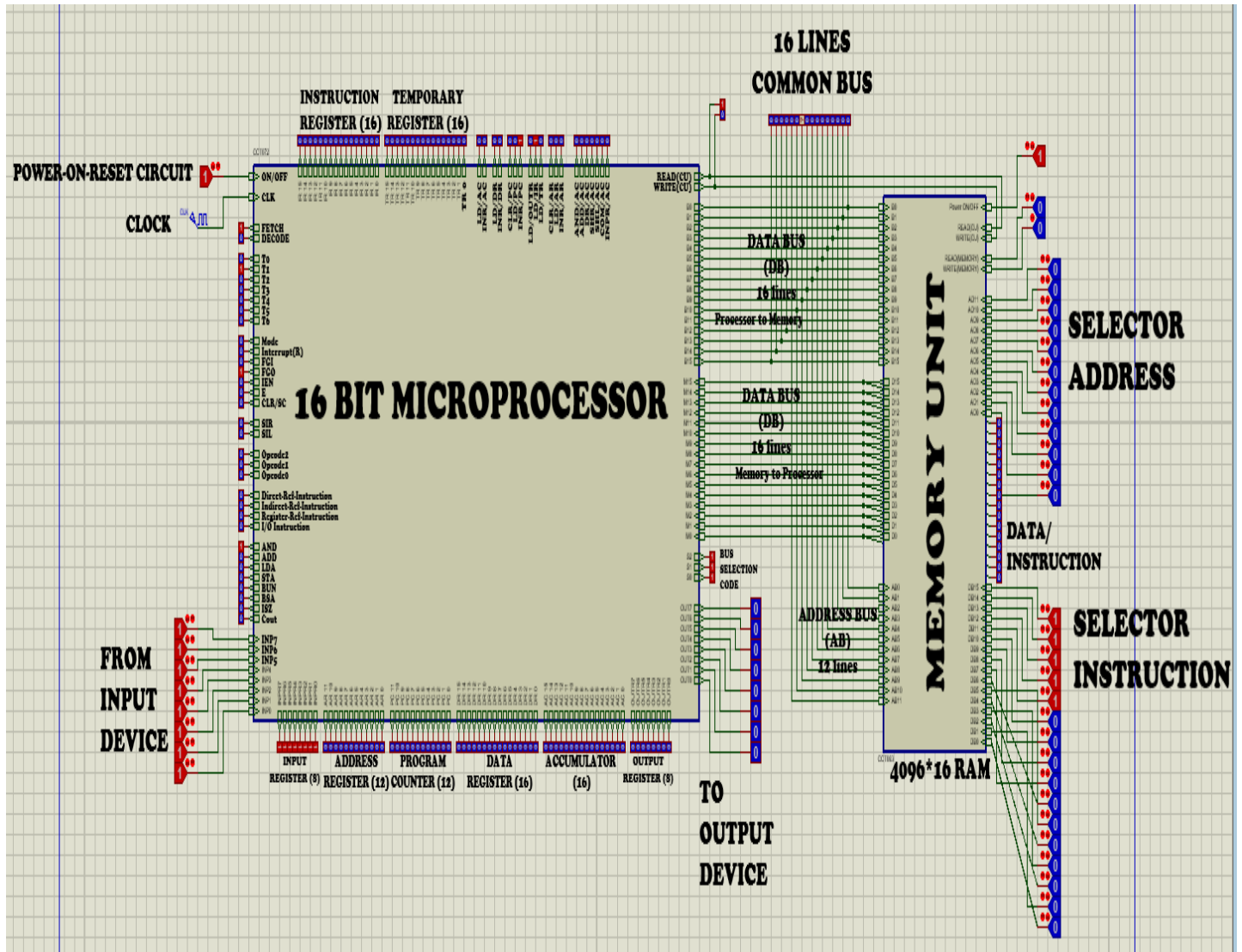

# INSTRUCTION SET

---

Fetch	$R' T_0:$	$AR \leftarrow PC$
	$R' T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R' T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$
Indirect	$D_7 IT_3:$	$AR \leftarrow M[AR]$
Interrupt:		
	$T_0 T_1' T_2' (IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0 T_4:$	$DR \leftarrow M[AR]$
	$D_0 T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \rightarrow 0$
ADD	$D_1 T_4:$	$DR \leftarrow M[AR]$
	$D_1 T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out} \rightarrow SC \leftarrow 0$
LDA	$D_2 T_4:$	$DR \leftarrow M[AR]$
	$D_2 T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3 T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4 T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5 T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5 T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6 T_4:$	$DR \leftarrow M[AR]$
	$D_6 T_5:$	$DR \leftarrow DR + 1$
	$D_6 T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then}$ $(PC \leftarrow PC + 1), \quad SC \leftarrow 0$
Register-reference:		
	$D_7 I' T_3 = r$	(common to all register-reference instructions)
	$IR(i) = B_i$	( $i = 0, 1, 2, \dots, 11$ )
	$r:$	$SC \leftarrow 0$
CLA	$rB_{11}:$	$AC \leftarrow 0$
CLE	$rB_{10}:$	$E \leftarrow 0$
CMA	$rB_9:$	$AC \leftarrow \overline{AC}$
CME	$rB_8:$	$E \leftarrow \overline{E}$
CIR	$rB_7:$	$AC \leftarrow \text{shr } AC, \quad AC(15) \leftarrow E, \quad E \leftarrow AC(0)$
CIL	$rB_6:$	$AC \leftarrow \text{shl } AC, \quad AC(0) \leftarrow E, \quad E \leftarrow AC(15)$
INC	$rB_5:$	$AC \leftarrow AC + 1$
SPA	$rB_4:$	If $(AC(15) = 0)$ then $(PC \leftarrow PC + 1)$
SNA	$rB_3:$	If $(AC(15) = 1)$ then $(PC \leftarrow PC + 1)$
SZA	$rB_2:$	If $(AC = 0)$ then $PC \leftarrow PC + 1$
SZE	$rB_1:$	If $(E = 0)$ then $(PC \leftarrow PC + 1)$
HLT	$rB_0:$	$S \leftarrow 0$
Input-output:		
	$D_7 IT_3 = p$	(common to all input-output instructions)
	$IR(i) = B_i$	( $i = 6, 7, 8, 9, 10, 11$ )
	$p:$	$SC \leftarrow 0$
INP	$pB_{11}:$	$AC(0-7) \leftarrow INPR, \quad FGI \leftarrow 0$
OUT	$pB_{10}:$	$OUTR \leftarrow AC(0-7), \quad FGO \leftarrow 0$
SKI	$pB_9:$	If $(FGI = 1)$ then $(PC \leftarrow PC + 1)$
SKO	$pB_8:$	If $(FGO = 1)$ then $(PC \leftarrow PC + 1)$
ION	$pB_7:$	$IEN \leftarrow 1$
IOF	$pB_6:$	$IEN \leftarrow 0$


---

# THE CONTROL UNIT

This is sometimes referred as the master of the computer processes because it lets the computer's logic unit, memory and both input and output devices know how to respond to instructions received from a program.

Instructions are fetched into the control unit which in turn decodes the instructions so that the **adder and logic circuit** can understand.

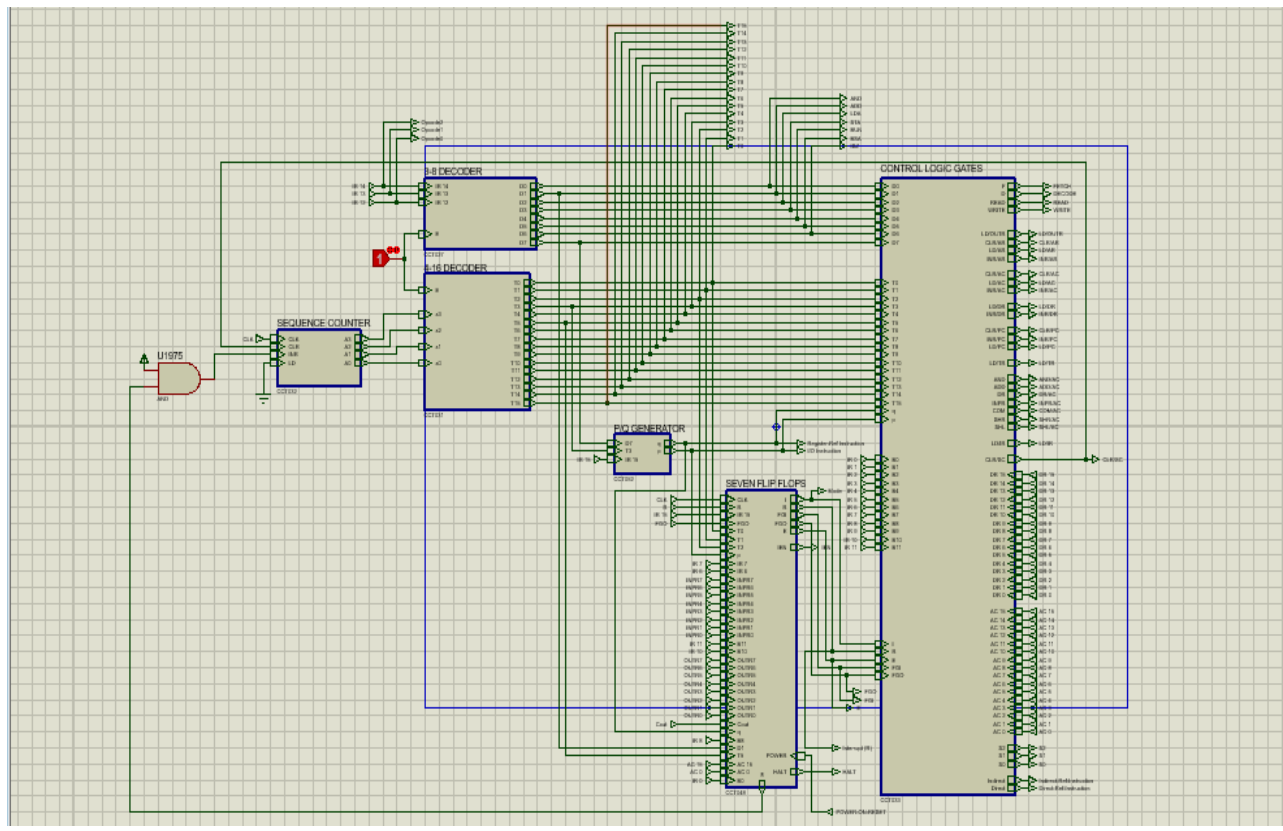As it can be seen below our control unit is made up of the control logic gates, 7-flipflops, PQ-generator, sequence counter, 4x16-decoder and the 3x8-decoder.




# The Control Logic Gates

This is a hardware component of a basic computer system, it comprises of inputs and outputs the diagram below shows hard wiring of the control organization.

Here, we have the 9 control logic gates for the 9 registers, fetch and decode process, the bus counter gates, the 7-flipflop as you can clearly observe below.

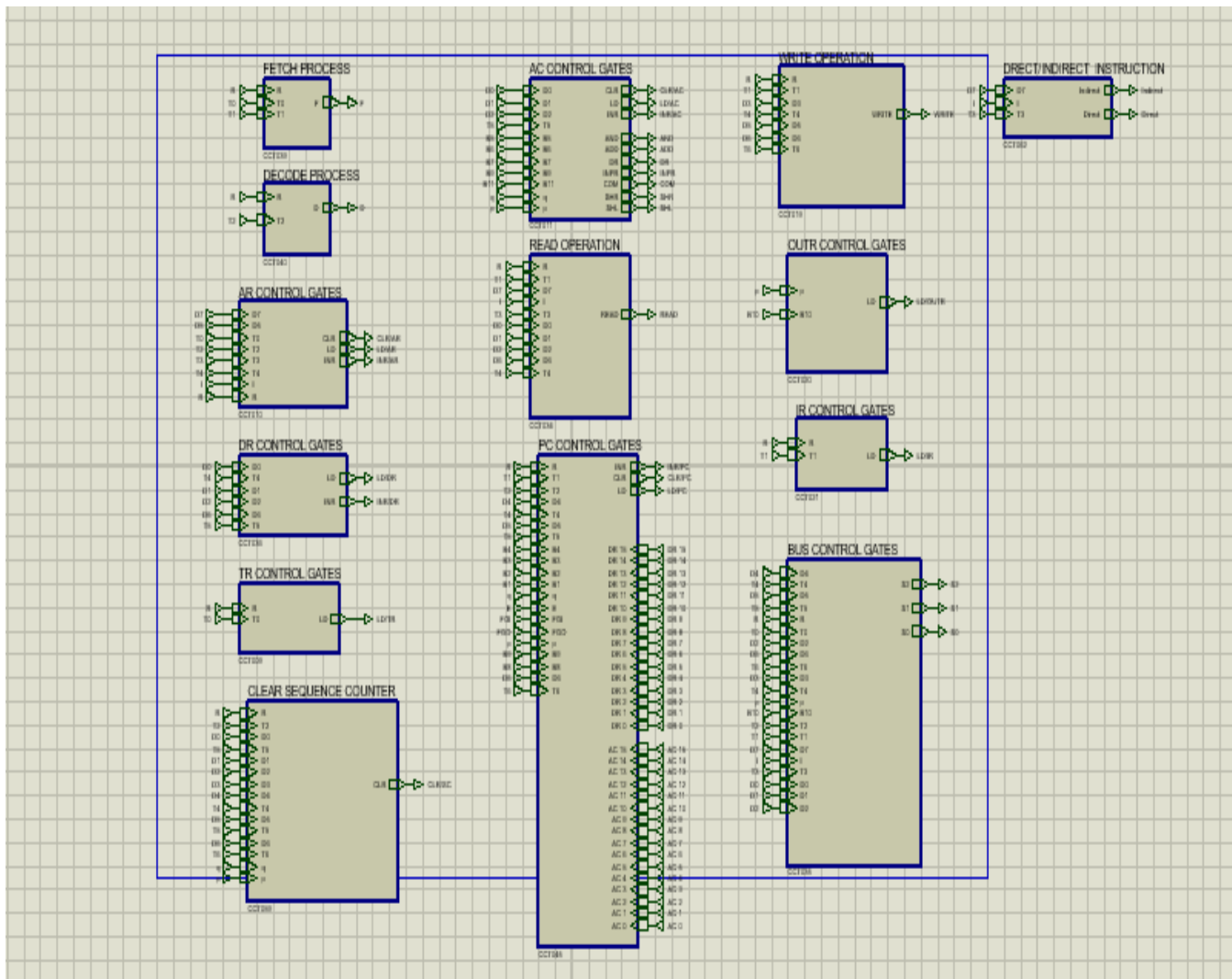The control logic gates get its inputs from the 3x8 decoder and the 4x16 decoder, the I-flip-flop, bits 0 through 11 of the instruction register.




# THE REGISTERS

This refers to a group of flip-flops with each flip-flop capable of storing one bit of information, this mean that an n-bit register has n-flip-flops and store n-bit of information. In this project, we shall focus on 9- registers which store their own amount of data and have different number of bits.

The memory address register (AR) has 12 bits since this is the width of a memory address. The program counter (PC) also has 12 bits and it holds the address of the next instruction to be read from memory after the current instruction is executed. The PC goes through a counting sequence and causes the computer to read sequential instructions previously stored in memory. Instruction words are read and executed in sequence unless a branch instruction is encountered. A branch instruction calls for a transfer to a nonconsecutive instruction in the program. The address part of a branch instruction is transferred to PC to become the address of the next instruction. To read an instruction, the content of PC is taken as the address for memory and a memory read cycle is initiated. PC is then incremented by one, so it holds the address of the next instruction in sequence. Two registers are used for input and output. The input register (INPR) receives an 8-bit character from an input device. The output register (OUTR) holds an 8-bit character for an output device.

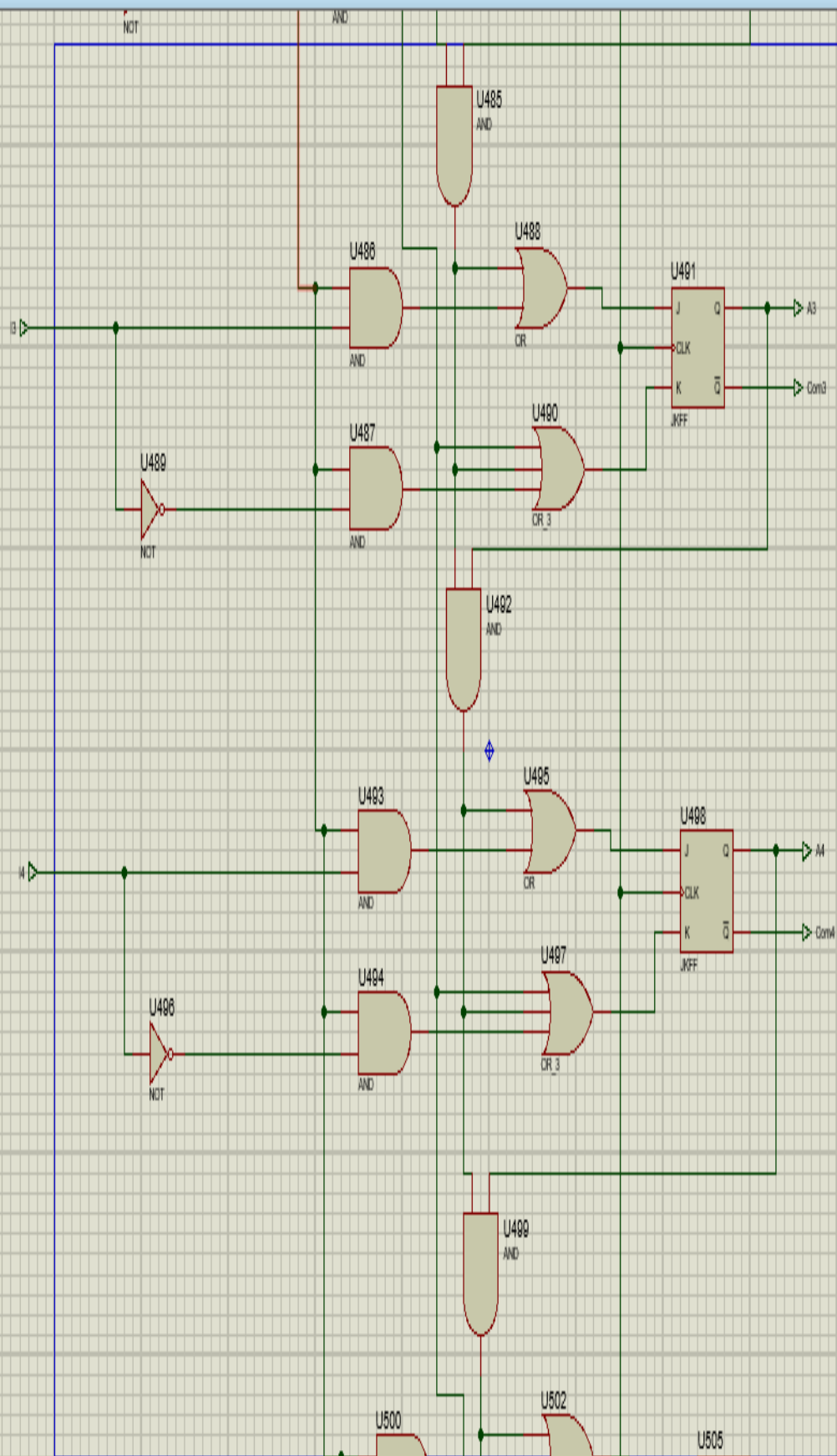As you can see in the diagram below which illustrates the 9 registers which all have the same circuit diagram but now differ in the number of bits which determines the number of times circuit will be repeated.






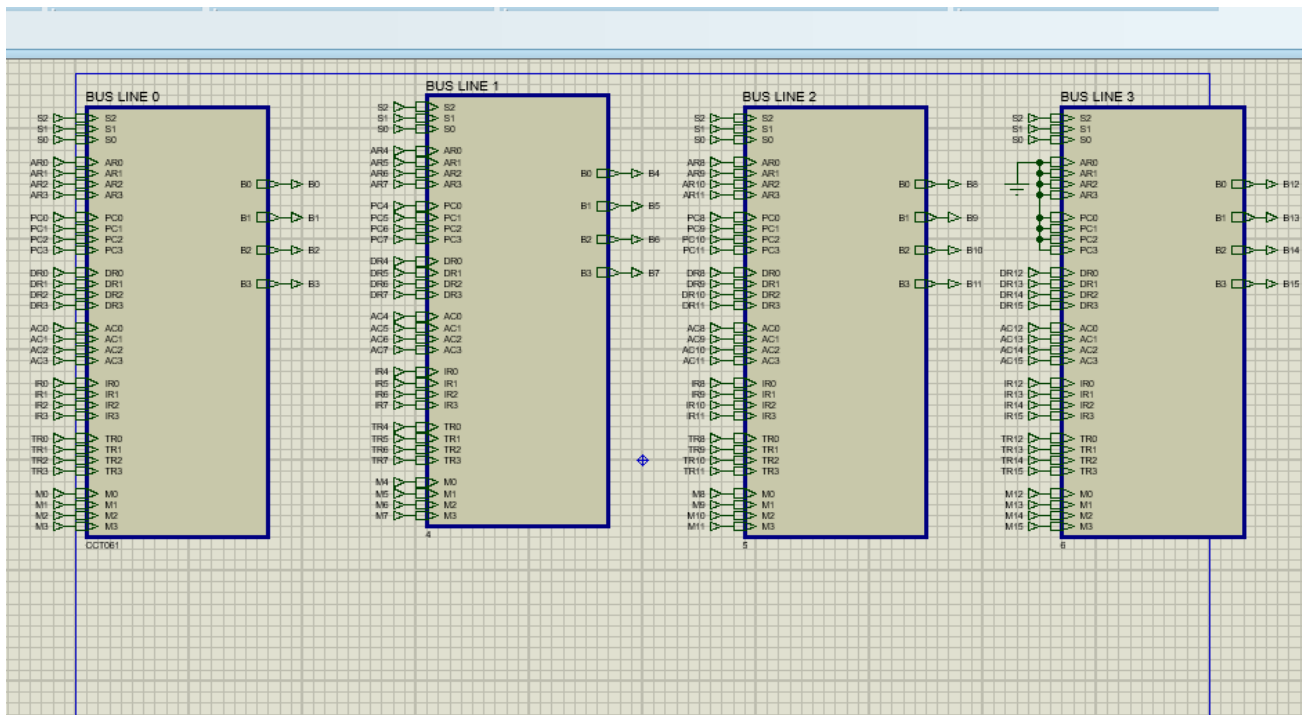
# THE BUS

A bus structure consists of a set of common lines, one for each bit of a register, through which binary information is transferred one at a time. Control signals determine which register is selected by the bus during each particular register transfer. One way of constructing a common bus system is with multiplexers. The multiplexers select the source register whose binary information is then placed on the bus. The construction of a bus system for eight registers is shown below. Each register has its own number of bits which ranges from 8-16 bits. The bus consists of sixteen 8x1 multiplexers with 3 selection inputs, S2, S1 and S0. In order not to complicate the diagram with 16 lines crossing each other, we use labels to show the connections from the outputs of the registers to the inputs of the multiplexers. The diagram shows that the bits in the same significant position in each register are connected to the data inputs of one multiplexer to form one line of the bus. Thus MUX 0 multiplexes the sixteen 0 bits of the registers, MUX 1 multiplexes the sixteen 1 bit of the registers, and similarly for the other two bits.


we have four bus which are bus line 0,1,2 and 3. In each bus line you find four 8x1 MUX giving us a total of sixteen 8x1 MUX as shown in the diagram



Content of one bus line

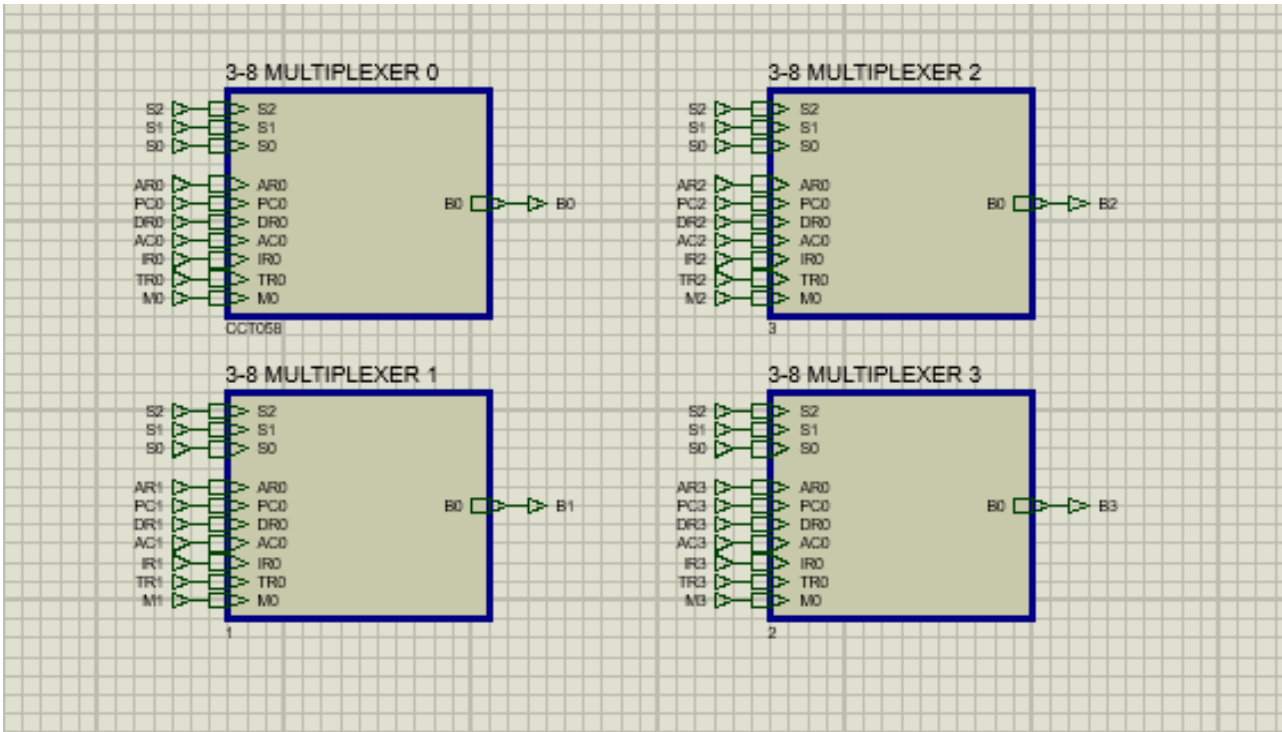


## 8x1-MUX

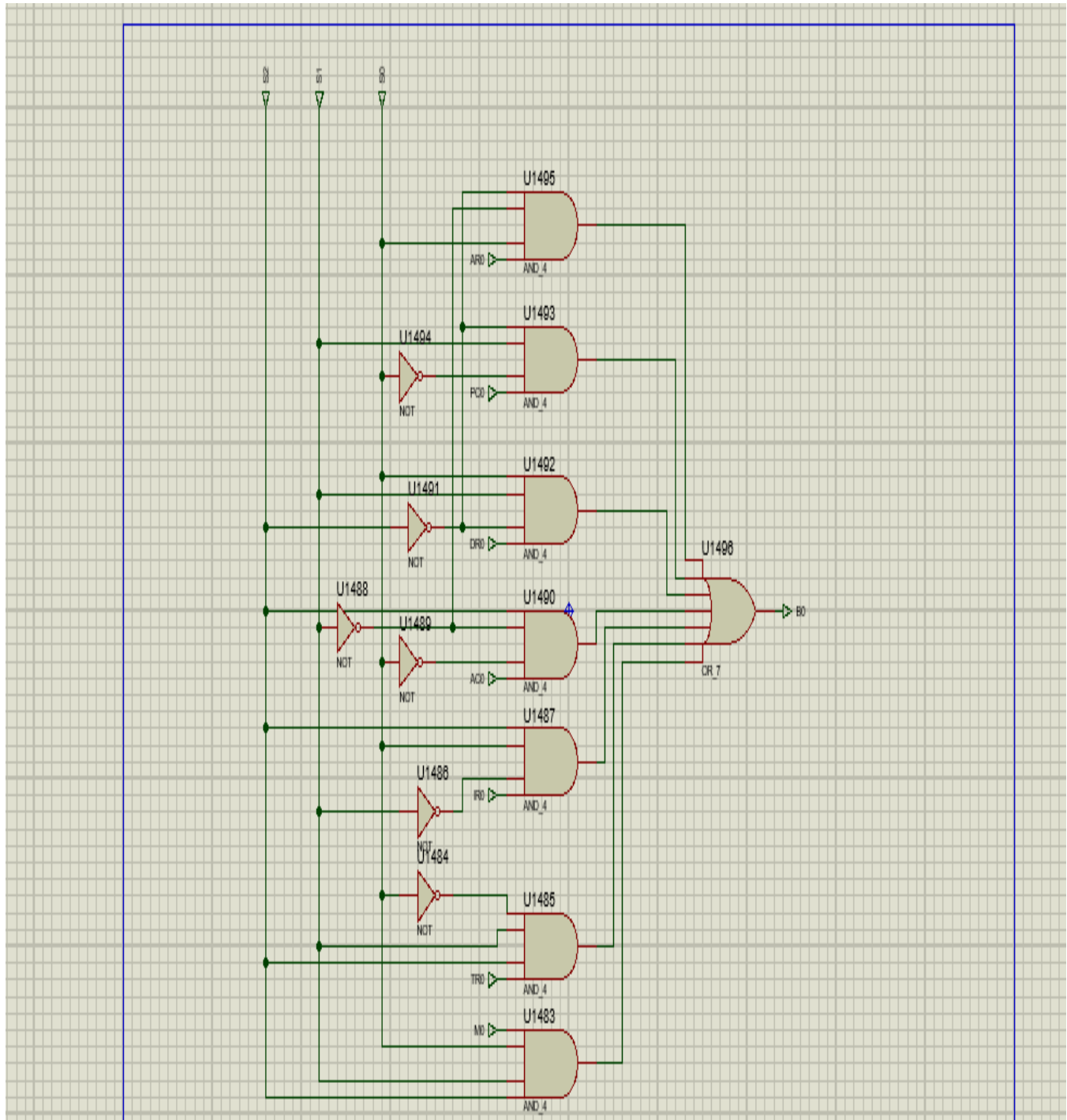
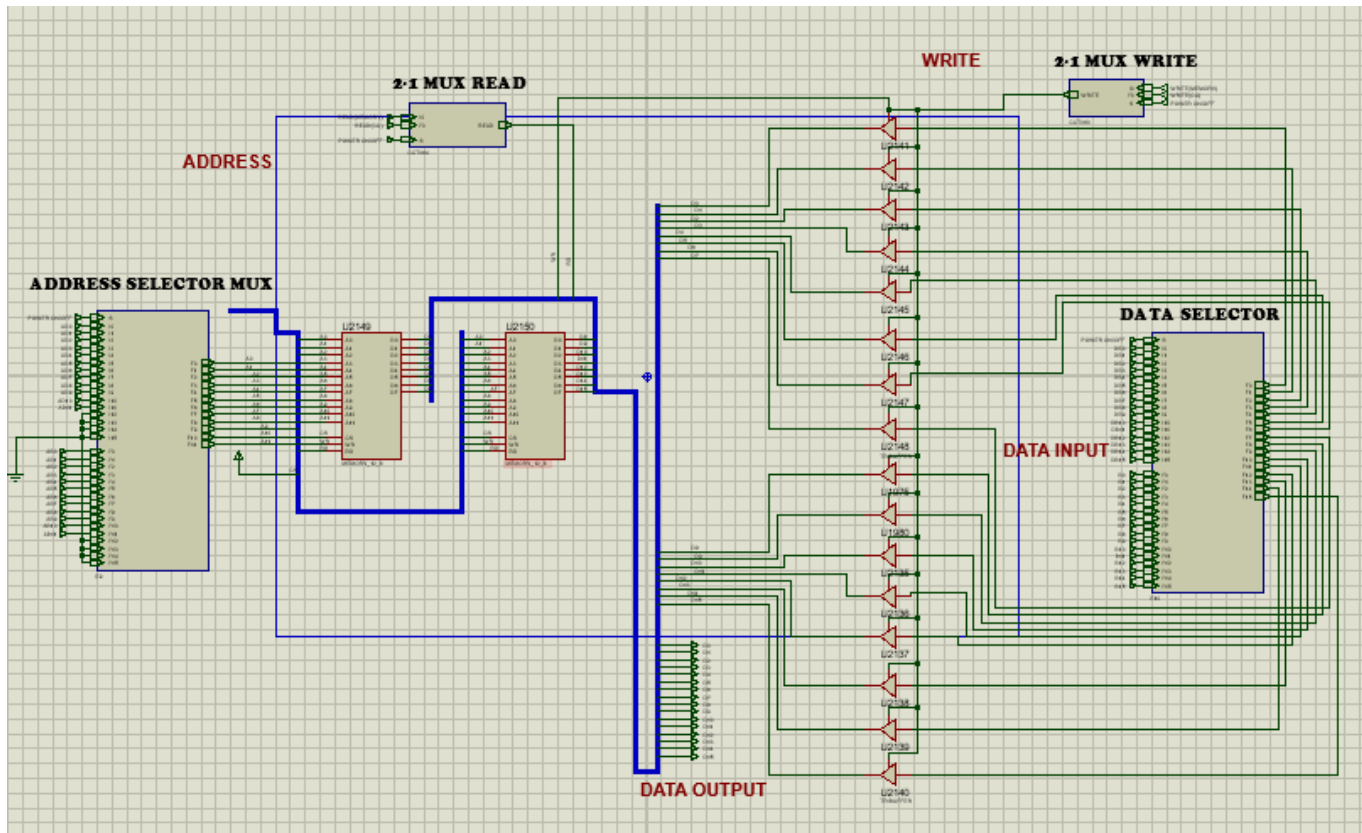
## **THE MEMORY**

The memory sometimes known as the storage unit of the computer is divided into the RAM and ROM in our case.

RAM and ROM chips are connected to a CPU through the data and address buses. The low-order lines in the address bus select the byte within the chips and other lines in the address bus select a particular chip through its chip select inputs. The connection of memory chips to the CPU. This configuration gives a memory capacity of 512 bytes of RAM and 512 bytes of ROM. Each RAM receives the seven low-order bits of the address bus to select one of 128 possible bytes. The particular RAM chip selected is determined from lines 8 and 9 in the address bus. This is done through a  $2^4$  decoder whose outputs go to the CS1 inputs in each RAM chip. Thus, when address lines 8 and 9 are equal to 00, the first RAM chip is selected. When 01, the second RAM chip is selected, and so on. The RD and WR outputs from the microprocessor are applied to the inputs of each RAM chip. The selection between RAM and ROM is achieved through bus line 10. The RAMs are selected when the bit in this line is 0, and the ROM when the bit is 1. The other chip select input in the ROM is connected to the RD control line for the ROM chip to be enabled only during a read operation. Address bus lines 1 to 9 are applied to the input address of ROM without going through the decoder. This assigns addresses 0 to 511 to RAM and 512 to 1023 to ROM. The data bus of the ROM has only an output capability, whereas the data bus connected to the RAMs can transfer information in both.



The adder and logic circuit can be subdivided into 16 stages, with each stage corresponding to one bit of AC. The internal construction of the register is as shown in Fig. 2-11. Looking back at that figure we note that each stage has a JK flip-flop, two OR gates, and two AND gates. The load (LD) input is connected to the inputs of the AND gates. Figure 5-22 shows one such AC register stage (with the OR gates removed). The input is labeled  $I_i$  and the output  $AC(i)$ . When the LD input is enabled, the 16 inputs  $I_i$  for  $i = 0, 1, 2, \dots, 15$  are transferred to AC (0–15). One stage of the adder and logic circuit consists of seven AND gates, one OR gate and a full-adder (FA), as shown in Fig. 5-22. The inputs of the gates with symbolic names come from the outputs of gates marked with the same symbolic name in Fig. 5-21. For example, the input marked ADD in Fig. 5-21 is connected to the output marked ADD in Fig. 5-21. The AND operation is achieved by ANDing  $AC(i)$  with the corresponding bit in the data register  $DR(i)$ . The ADD operation is obtained using a binary adder similar to the one shown in Fig. 4-6. One stage of the adder uses a full-adder with the corresponding input and output carries. The transfer from INPR to AC is only for bits 0 through 7. The complement microoperation is obtained by inverting the bit value in AC. The shift-right operation transfers the bit from AC ( $i + 1$ ), and the shift-left operation transfers the bit from AC ( $i$

- 
- 1). The complete adder and logic circuit consists of 16 stages connected together. The diagram below illustrates the circuit diagram of the adder and logic circuit.

